

CSCI 2461: Lab 1

- Introductions
- Review Binary Representation
- Quick Physics Review

1

Who are we ?

- Sam Kusner
- Kate Halushka
- Karl Simon

- Ruining Yang

- Lauren Hahn
- Jonathan Lee

2


**What to expect in this course ?
Our experience**

3

Today's Lab session

- 1. Review lecture on Binary RepresentationQuestions ?
- 2. Quick review of Physics (needed for circuit design)

4

 

5


(Unsigned) Integer Representation

- Non-positional notation (unary): 5 represented as 11111
- What are you used to ? Decimal representation (0..9) and...
- Decimal **Weighted positional representation**
 - *Position gives the weight of the location*
- Extend to any base, including binary.....
 - Weights in decimal are $10^0, 10^1, 10^2, 10^3, \dots$
 - Weights in binary are $2^0, 2^1, 2^2, 2^3, \dots$

6

Integer Representation

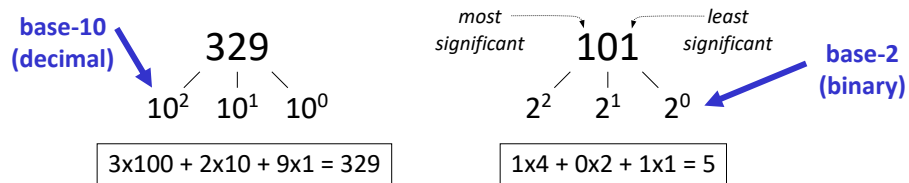- Weighted positional representation in Binary



Notations: the bit position i has weight of 2^i

n bit binary number $a_{n-1}a_{n-2}, \dots, a_1, a_0$

represents the decimal value/number

$$\sum_{i=0}^{i=n-1} a_i 2^i$$

7

Questions

- what decimal number does the binary string 11001 represent
- What decimal number does 00110 represent ?

8

Decimal to Binary Conversion:

1. What is the binary representation of decimal number 19

- Express 19 as a sum of numbers each a power of 2
- Algorithm to convert decimal (base 10) to binary (base 2)
 - Generalize to convert from base k to base m

k bit number: $b_{k-1}, b_{k-2}, \dots, b_1, b_0$

Decimal integer N represented by this binary number is:

$$b_{k-1} 2^{k-1} + b_{k-2} 2^{k-2} + \dots + b_1 2^1 + b_0 2^0$$

$$\begin{aligned} 19 &= 1 \cdot 16 + 0 \cdot 8 + 0 \cdot 4 + 1 \cdot 2 + 1 \cdot 1 \\ &= \mathbf{1} \cdot 2^4 + \mathbf{0} \cdot 2^3 + \mathbf{0} \cdot 2^2 + \mathbf{1} \cdot 2^1 + \mathbf{1} \cdot 2^0 \\ &10011 \end{aligned}$$

9

Conversion from Decimal to Binary

//input is Decimal number N, output is list of bits b_i //

$i=0$;

while $N > 0$ do

$b_i = N \% 2$; // $b_i =$ remainder; $N \bmod 2$

$N = N / 2$; // N becomes quotient of division

$i++$;

end while /* replace 2 by k and your algo can convert to any base k */

- Iteration $i=0$: $b_0 = 19 \% 2 = 1$ and $N = 19 / 2 = 9$
- Iteration 1: $b_1 = 9 \% 2 = 1$ and $N = 4$
- Iteration 2: $b_2 = 4 \% 2 = 0$ and $N = 2$
- Iteration 3: $b_3 = 2 \% 2 = 0$ and $N = 1$
- Iteration 4: $b_4 = 1 \% 2 = 1$ and $N = 0$ so loop terminates
- Binary representation of 19 = 10011

10

Questions

- What is the binary representation of 11

- What is the binary representation of 23

11

Quick Physics Review

Why ? we need a bit of this to study digital logic circuits


- Basics of electricity:
 - Voltage
 - Current
 - Resistance

- Ohm's law

12

Let's start with a river....


- Water always flows from high elevation to low elevation
- Speed of the water flow is dependent on:
 - Steepness of the slope/height of the source
 - Obstructions in the river's path that resist the flow of water
- The height difference is a type of "potential" energy
 - Higher the start of the river the greater the flow/pressure
 - A **voltage** difference analogous to an elevation difference in a waterfall – water flows from higher elevation to lower elevation

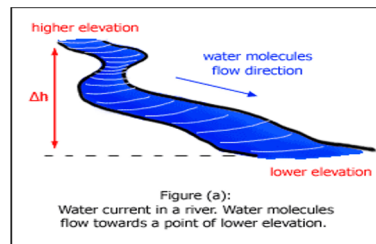

13

Voltage


- Measured in Volts – symbol for voltage is V
- Always measure relative to some baseline (usually "ground" or 0 volts)
- Battery is most common source of voltage
 - Analogous to a "pump" that releases electricity into a circuit at a certain voltage (potential/ height)
- Conventionally, electricity moves from high voltage (+ve) to low voltage (-ve)
 - Electrons flow from -ve to +ve
- A **voltage** difference between 2 points captures the amount of work it would take to move charge from one point to another
 - analogous to an elevation difference in a waterfall

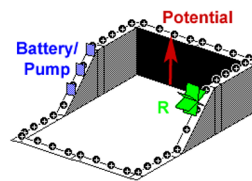

14

Current and Resistance

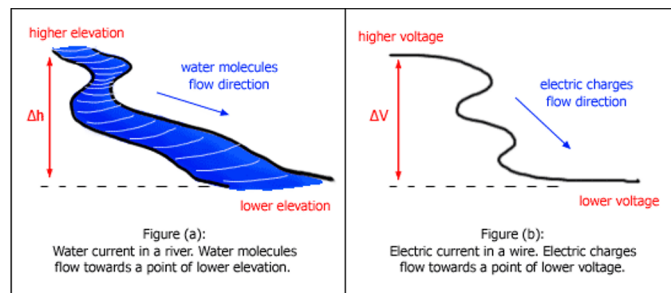- Current: A measurement of the flow of electricity, i.e., “how fast” it’s going
 - Flow of electrons
 - Measured in Amperes (amps) – symbol is I
- Resistance: opposes the flow (of electricity)
 - Measured in Ohm’s – symbol is R
 - Resistor = common electrical component that offers resistance in circuit



15

Ohm’s Law

- Voltage, Current, Resistance in a circuit are closely related
 - More voltage = more current flow
 - More resistance = less current flow
 - But we can add voltage to increase current !
- Ohm’s Law: formula to describe the voltage-current-resistance relationship


$$V = I \cdot R$$

- You can also solve
- current $I = V/R$
- Resistance $R = V/I$
- Note if R is infinity (very large) then current = 0 !

16


Voltage/Current and Electric Field

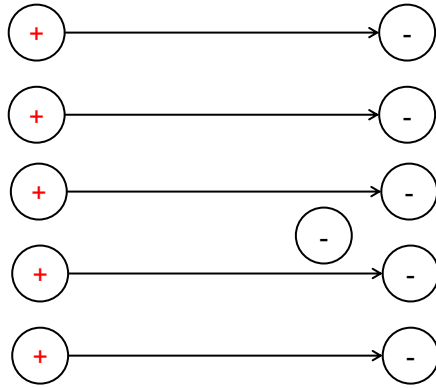E-field produces "potential difference"
Aka: motivation for charge to flow



← Direction of charge carrier (e-)
→ Direction of current

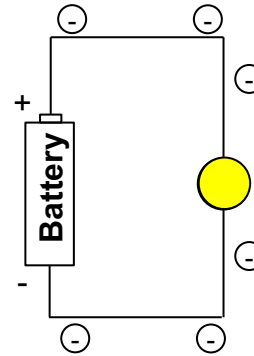Battery provide voltage
Aka: potential difference




← Direction of current
Ohm's Law: $V = IR$


17

Looking at a circuit diagram

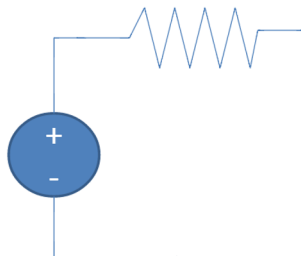- Do we know which way the electricity flows ?




*Usual symbol for battery:

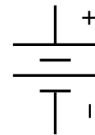

18

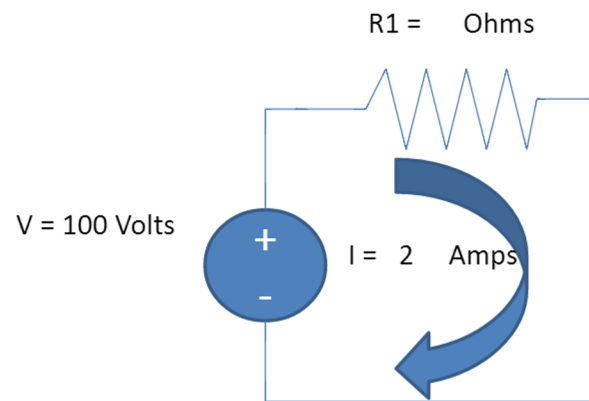Example Problem 1:


- What is the value of R_1 ?
- Recall Ohm's law $V = IR$



19

Example Problem 2

- What is the value of V ?

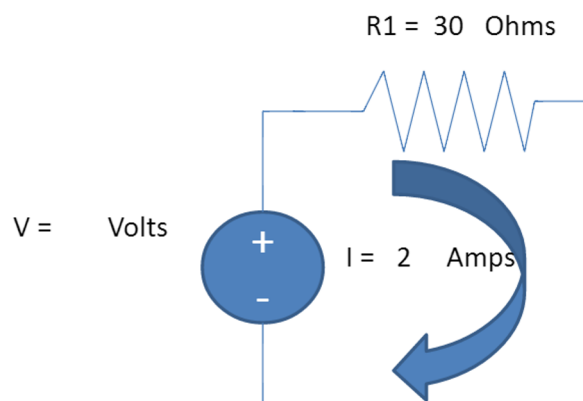

20


More circuit theory.....

- Types of Circuits
 - Series
 - Parallel

21

What is a “series” circuit ?

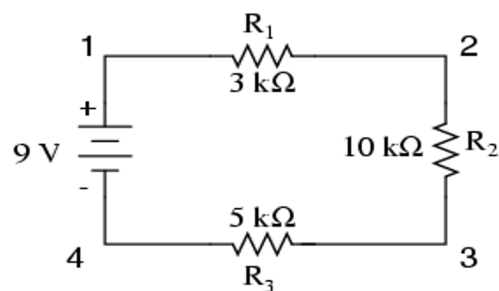- When components are placed one after another (ex: some Christmas lights)
- Characteristic: the current at all points will be the same
 - $I_1 = I_2 = I_3$
 - Electricity does not “build up” in front of R_1 because the current is slowed to the same speed at all points



22

“Series” circuits

- Voltage sources in series are added together
 - $2 * 1.5 = 3.0V$




- ..and so do resistances

$$\text{Series: } \begin{array}{c} R_1 \\ \text{---} \end{array} \begin{array}{c} R_2 \\ \text{---} \end{array} \begin{array}{c} R_3 \\ \text{---} \end{array} = \begin{array}{c} R_{eq} = R_1 + R_2 + R_3 \\ \text{---} \end{array}$$

23

What is a “parallel” circuit

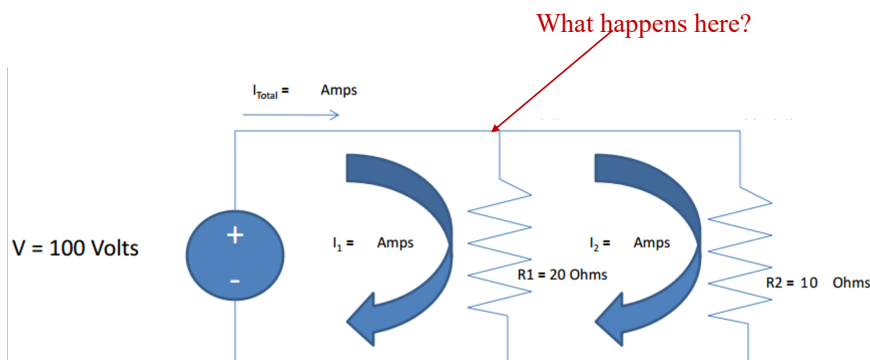
- Anytime we have multiple paths for electricity to follow (i.e., forks in the road!)
- So, we need to know how forks affect our voltage and current....



24

Path of least resistance


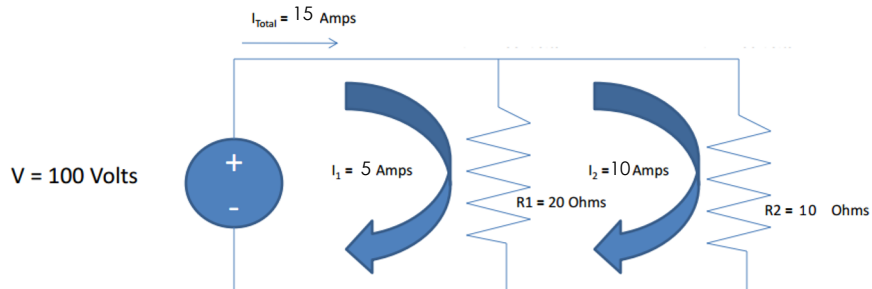
- Current flowing through each branch is proportional to the resistance
 - i.e., we see more current (double) flowing through R_2 than R_1
- *Question: What if $R_1 = \text{infinity}$? Does any current flow through it*



25

Switches (very relevant to us!)

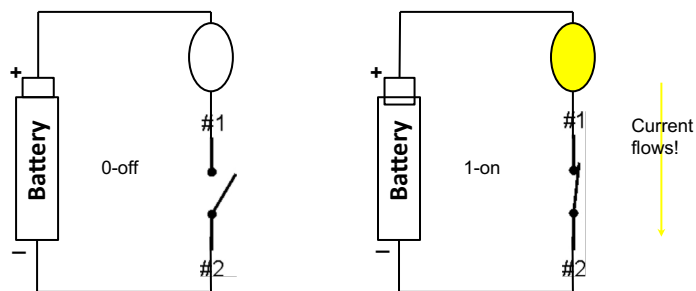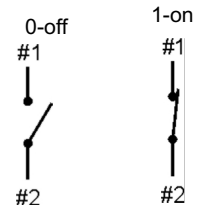- A switch inherently represents two states: ON/OFF (closed/open)
 - Interpret ON=1 and OFF=0 and we have binary!
- When switches are put in a circuit, can start/stop current flow




26

Switches and Series/Parallel Circuits


- Putting multiple switches in a circuit (replace resistors with switches)

Switches are in series

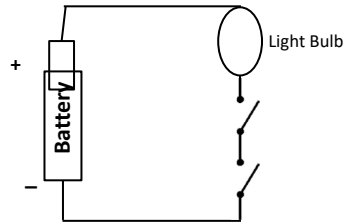

Both switches must be "on" for bulb to light up (AND)

Switches are in Parallel

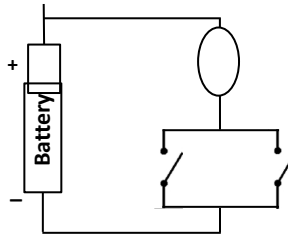


Only 1 switch must be "on" for Bulb to light up (OR)

27


Switches and Series/Parallel Circuits

Switches are in series

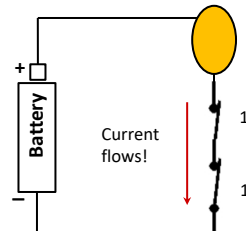

Both switches must be "on" for current to flow from + to - (for bulb to light up) (AND)

Switches are in Parallel

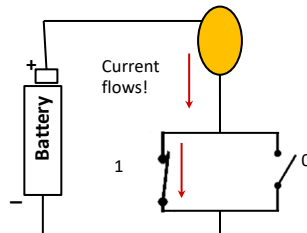

Only 1 switch must be "on" for current to flow from + to - (for bulb to light up) (OR)

28

Series & Parallel Circuits: Key takeaway

- Series circuits: resistance adds up and there is still only one path from +ve to -ve.
- Current flows through each of the parallel circuits from Voltage source (battery +) to voltage ground (battery - ve).
 - More current flows through circuit with lower resistance...path of least resistance!!
- In context of switches (instead of resistors):
 - **Parallel Circuits: Current flows if at least one of the switches is closed/ON**
 - No current flows if ALL switches are open/OFF
 - **Series Circuits: Current flows if ALL switches are ON**
 - No current flows if at least one switch is OFF

29

Questions ?

30